



Atividade – Aula 18/03

ALUNO(A): GUILHERME LUCAS PEREIRA BERNARDO

ATENÇÃO: Vale ressaltar que esta atividade será utilizada como critério para a contabilização de sua frequência de aula.

PRAZO DE ENTREGA: 22/03/2021

[Questão – 01] Implemente os componentes abaixo usando a linguagem VHDL, para cada componente apresenta os testes do componente, apresentando o resultado dos pinos de entrada e saída.

[COMPONENTE 01]. Multiplexador de quatro opções de entrada.

CÓDIGO VHDL DO MULTIPLEXADOR4TO1:

```
library ieee;
use ieee.std_logic_1164.all;

entity mult is
    port(
        in_port : in STD_LOGIC_VECTOR(1 downto 0);
        in_portA : in STD_LOGIC_VECTOR(1 downto 0);
        in_portB : in STD_LOGIC_VECTOR(1 downto 0);
        in_portC : in STD_LOGIC_VECTOR(1 downto 0);
        in_portD : in STD_LOGIC_VECTOR(1 downto 0);
        out_port : out STD_LOGIC_VECTOR(1 downto 0);
    );
end mult;

architecture behavior of mult is
begin
    process (in_port, in_portA, in_portB, in_portC, in_portD)
    begin
        case in_port is
            when "00" => out_port <= in_portA;
            when "01" => out_port <= in_portB;
            when "10" => out_port <= in_portC;
            when "11" => out_port <= in_portD;
        end case;
    end process;
end behavior;
```

REPRESENTAÇÃO RTL

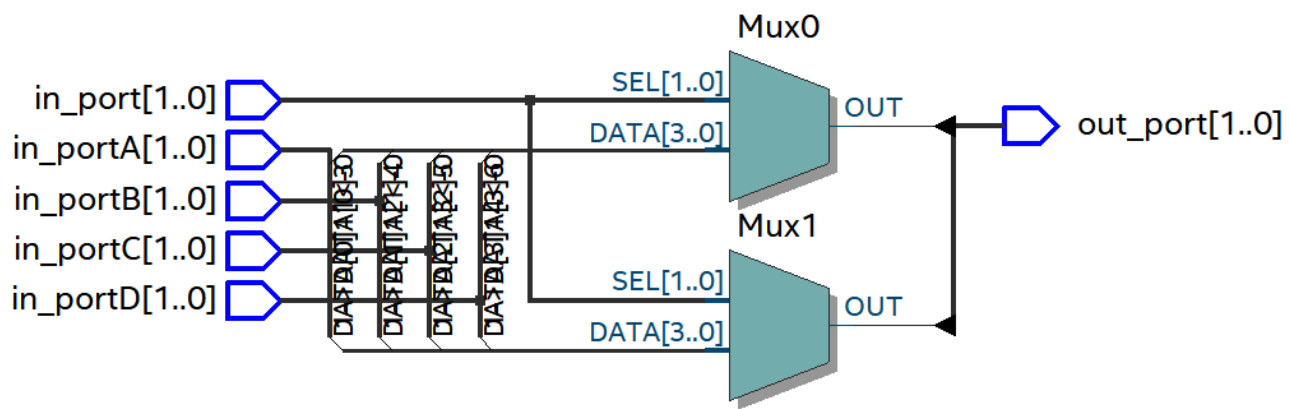


TABELA DE EXECUÇÃO DO MULTIPLEXADOR

> in_port	B 00	00	01	10	11
> in_portA	B 00	00	01	10	11
> in_portB	B 01	01	10	11	00
> in_portC	B 10	10	11	00	01
> in_portD	B 11	11	00	01	10
> out_port	B 00	00	10	00	10

LEGENDA:
quando in_port apresenta 00... out_port tem sinal igual a in_portA.
quando in_port apresenta 01... out_port tem sinal igual a in_portB.
quando in_port apresenta 10... out_port tem sinal igual a in_portC.
quando in_port apresenta 11... out_port tem sinal igual a in_portD.

[COMPONENTE 02]. Porta lógica XOR.

CÓDIGO VHDL DO P_XOR:

```
library ieee;
use ieee.std_logic_1164.all;

entity p_xor is
    port(
        in_portA : in STD_LOGIC;
        in_portB : in STD_LOGIC;
        out_port  : out STD_LOGIC
    );
end p_xor;

architecture behavior of p_xor is
begin
    out_port <= in_portA xor in_portB;
end behavior;
```

```
library ieee;
use ieee.std_logic_1164.all;

entity p_xor is
    port(
        in_portA : in STD_LOGIC;
        in_portB : in STD_LOGIC;
        out_port  : out STD_LOGIC
    );
end p_xor;

architecture behavior of p_xor is
begin
    out_port <= in_portA xor in_portB;
end behavior;
```

REPRESENTAÇÃO RTL

 


TABELA DE EXECUÇÃO DO P_XOR

	Name	Value at 0 ps	0 ps	10.0 ns	20.0 ns	30.0 ns	40.0 ns
in	in_portA	B 0	0	1	0	1	0
in	in_portB	B 0	0	0	1	0	1
out	out_port	B 0	0	1	0	1	0

LEGENDA:

out_port é igual a 1 se e somente se in_portA e in_portB forem igual a 1, fora isso a porta out_port é sempre 0.

[COMPONENTE 03]. Somador de 16 bits.

CÓDIGO VHDL DO SOMADOR16:

```
library ieee;
use ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;

entity somador16 is
    port(
        in_portA : in STD_LOGIC_VECTOR(15 downto 0);
        in_portB : in STD_LOGIC_VECTOR(15 downto 0);
        out_port : out STD_LOGIC_VECTOR(15 downto 0)
    );
end somador16;

architecture behavior of somador16 is
begin
    out_port <= in_portA + in_portB;
end behavior;
```

REPRESENTAÇÃO RTL

 


TABELA DE EXECUÇÃO DO SOMADOR16:

	Name	Value at 0 ps	0 ps	40,0 ns	80,0 ns	120,0 ns	160,0 ns	200,0 ns	240,0 ns	280,0 ns	320,0 ns	360,0 ns	400,0 ns	440,0 ns
in	> in_portA	B 00000000...	0000000000000000	0000000000000000	0000000000000001	0000000000000010	0000000000000011	0000000000000100	0000000000000101	0000000000000110	0000000000000111	0000000000001000	0000000000001001	0000000000001010
in	> in_portB	B 00000000...	0000000000000001	0000000000000010	0000000000000011	0000000000000100	0000000000000101	0000000000000110	0000000000000111	0000000000001000	0000000000001001	0000000000001010	0000000000001011	0000000000001100
out	> out_port	B 00000000...	0000000000000001	0000000000000010	0000000000000011	0000000000000100	0000000000000101	0000000000000110	0000000000000111	0000000000001000	0000000000001001	0000000000001010	0000000000001011	0000000000001100

LEGENDA:

out_port é o resultado da soma dos dois in_ports, no primeiro ciclo soma-se 0000000000000000 + 0000000000000001, no próximo ciclo realiza a soma 0000000000000001 + 0000000000000010 e por aí vai

[COMPONENTE 04]. Extensor de sinal de 8 bits para 16 bits.

CÓDIGO VHDL DO EXTENDER8TO16:

```
library ieee;
use ieee.std_logic_1164.all;

entity extender8to16 is
    port (
        in_port : in std_logic_vector(7 downto 0);
        out_port : out std_logic_vector(15 downto 0)
    );
end extender8to16;

architecture behavior of extender8to16 is
begin
    process (in_port)
    begin
        out_port <= ("00000000") & in_port;
    end process;
end behavior;
```

REPRESENTAÇÃO RTL:

 


TABELA DE EXECUÇÃO DO EXTENDER8TO16:

	Name	Value at 0 ps	0 ps	20,0 ns	40,0 ns	60,0 ns	80,0 ns	100,0 ns	120,0 ns	140,0 ns	160,0 ns	180,0 ns	200,0 ns	220,0 ns	240,0 ns
in	> in_port	B 00000000	00000000	00000001	00000010	00000011	00000100	00000101	00000110	00000111	00001000	00001001	00001010	00001011	00001100
out	> out_port	B 00000000...	0000000000000000	0000000000000001	0000000000000010	0000000000000011	0000000000000100	0000000000000101	0000000000000110	0000000000000111	0000000000001000	0000000000001001	0000000000001010	0000000000001011	0000000000001100

LEGENDA:

conversor simples de binário de 8 bits para 16 onde os números em 8bit de “in_port” são transferidos para “out_port” que é STD_LOGIC_VECTOR que comporta 16 bits

[COMPONENTE 05]. Contador Síncrono.

CÓDIGO VHDL DO UPCOUNTER:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.all;
use IEEE.STD_LOGIC_UNSIGNED.all;

entity upcounter is
    Port ( rst,clk : in std_logic;
          o: out std_logic_vector(0 to 3));
end upcounter;

architecture count_arch of upcounter is
    signal count : std_logic_vector(0 to 3);
    begin
        process(rst,clk)
        begin
            if (rst = '1') then count <= "0000";
            elsif (clk'event and clk = '1') then count <= count + 1;
            end if;
        end process;
        o <= count;
    end count_arch;
```

REPRESENTAÇÃO RTL:


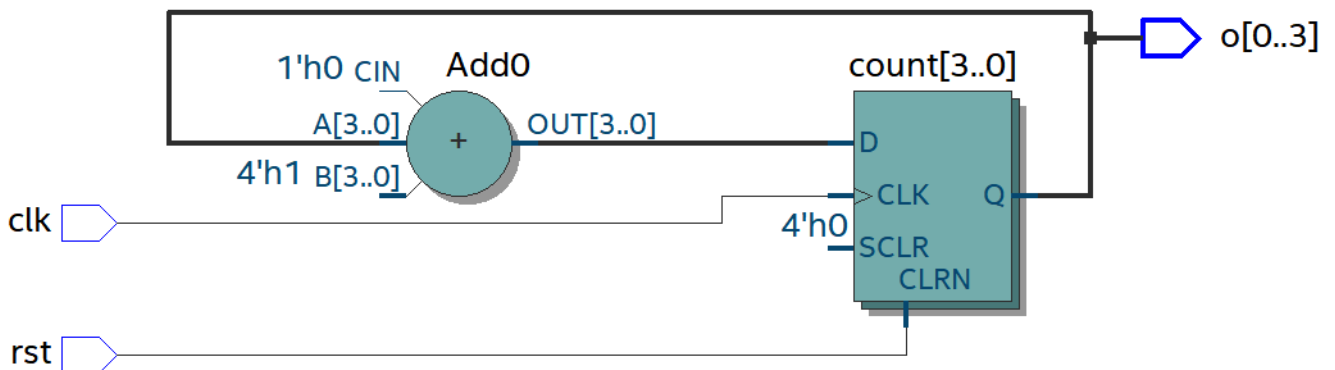


TABELA DE EXECUÇÃO DO UPCOUNTER:

 

LEGENDA:

Sendo “clk” o clock e “rst” o reset, a cada ciclo de clock de “clk”, “o” que é o contador é incrementado em 1, até um total de “1111”.

Toda vez que “rst” recebe 1, o contador “o” é resetado de volta para “0000” e enquanto “rst” for 1, “o” continuará nesse estado.

